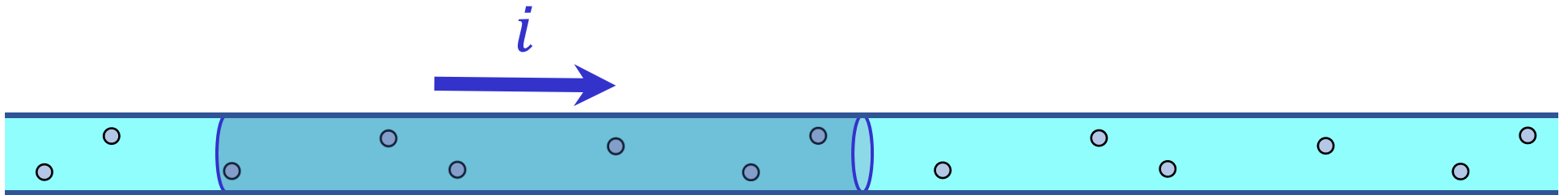


# Basic Introduction to Electronics






Electrical current

Symbol:  $i$

Unit: Ampere (A)

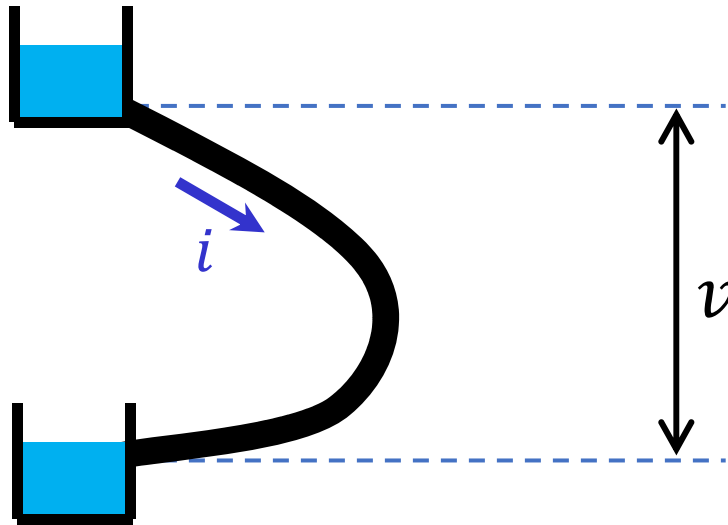For example:  $1 \text{ mA} = 0.001 \text{ Amperes}$




Voltage




Symbol:  $v$

Unit: Volt (V)

For example: 5 V


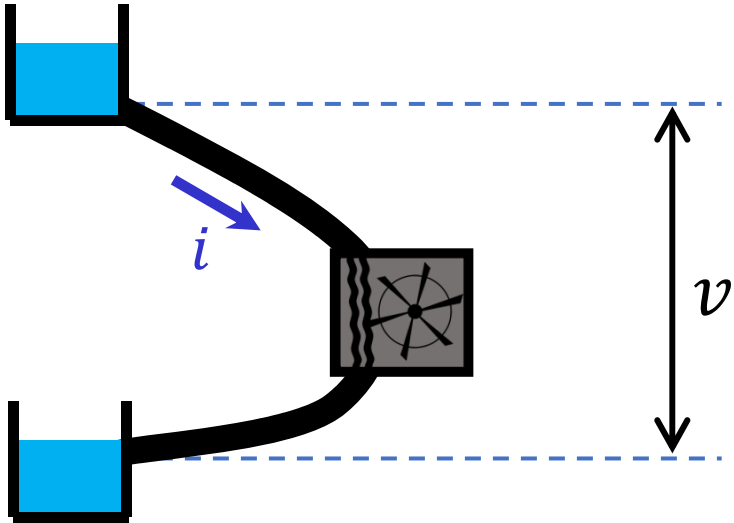


Circuit elements

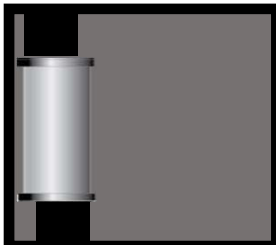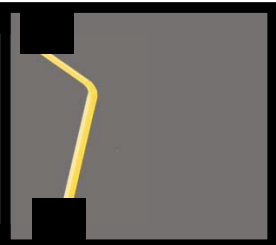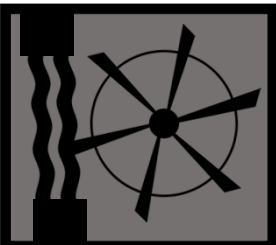


Same  $v$


Different  $i$

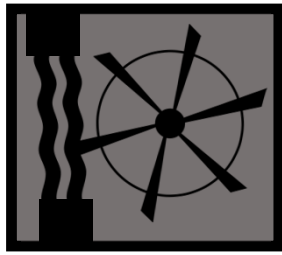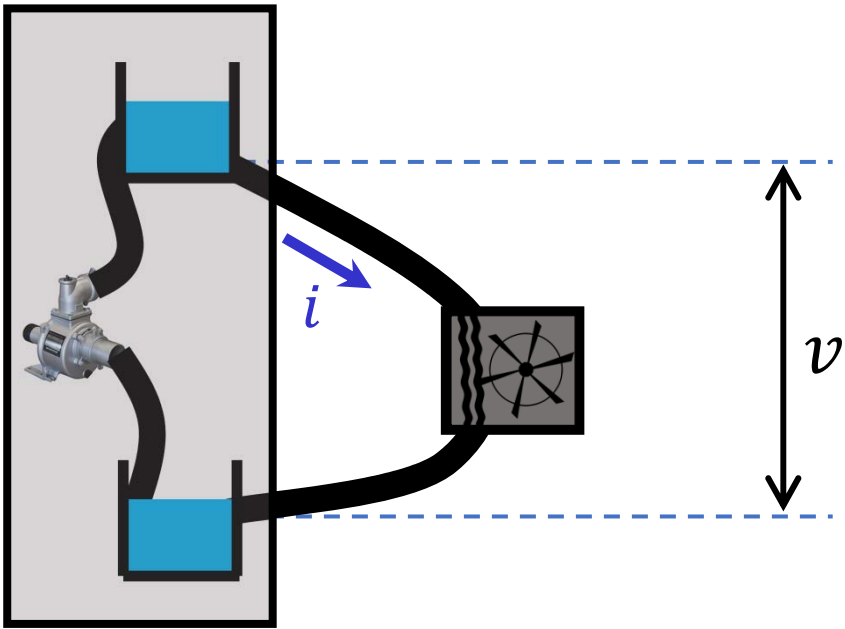


Same  $v$

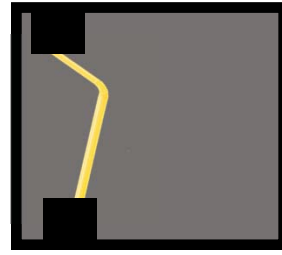

Different  $i$

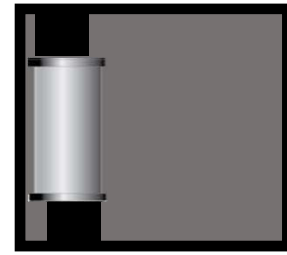



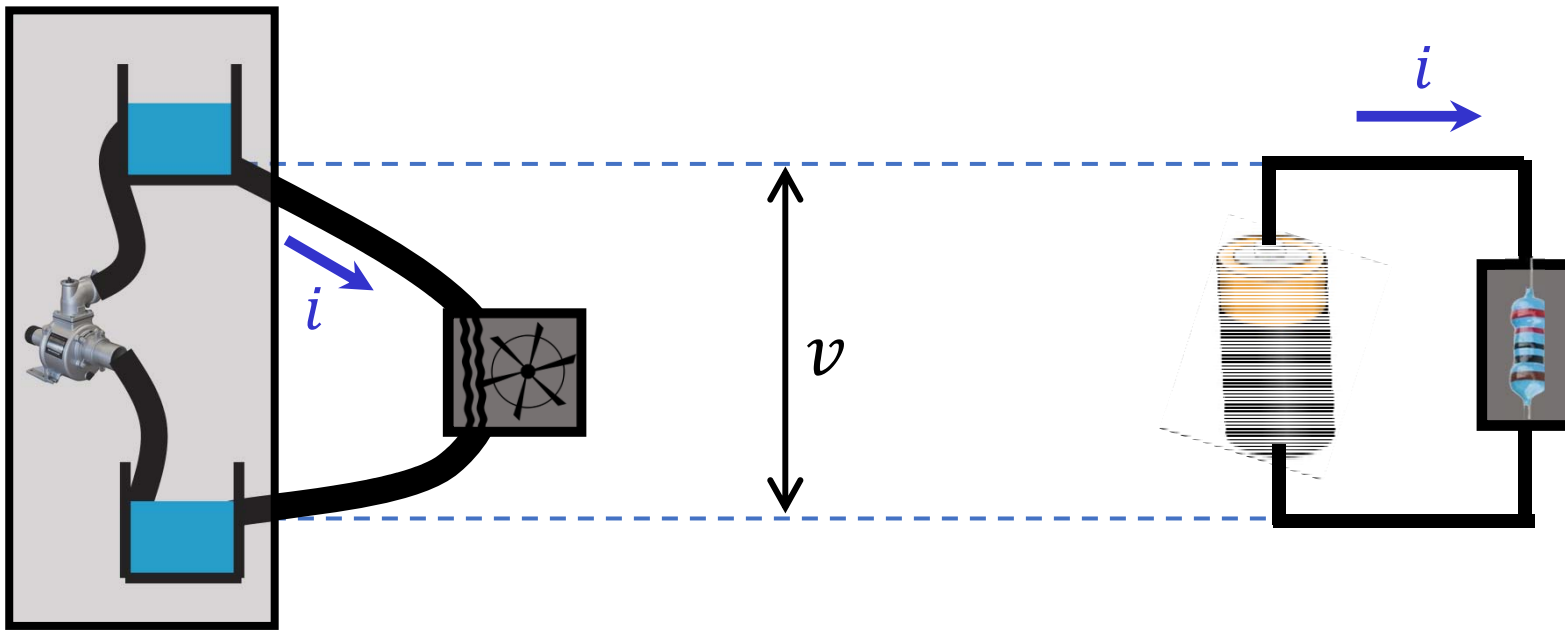


## Circuit elements







Same  $v$

Different  $i$

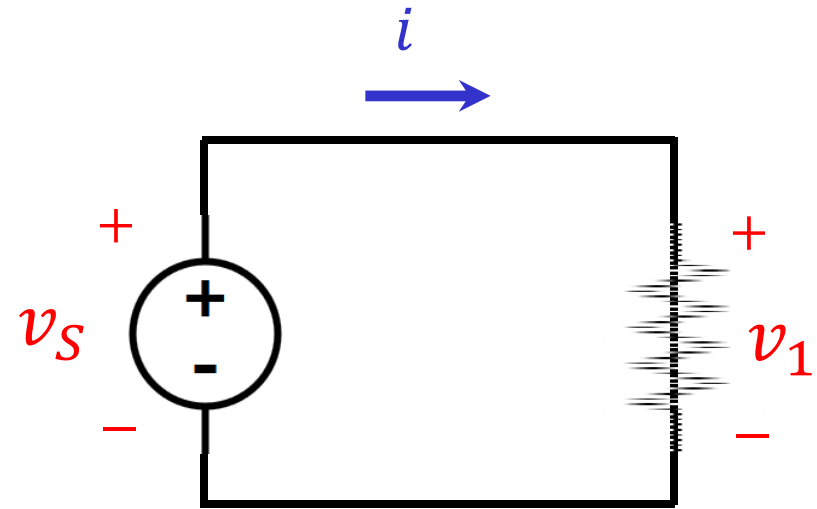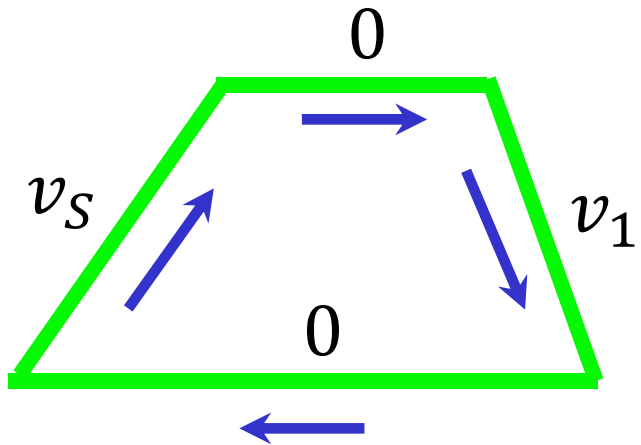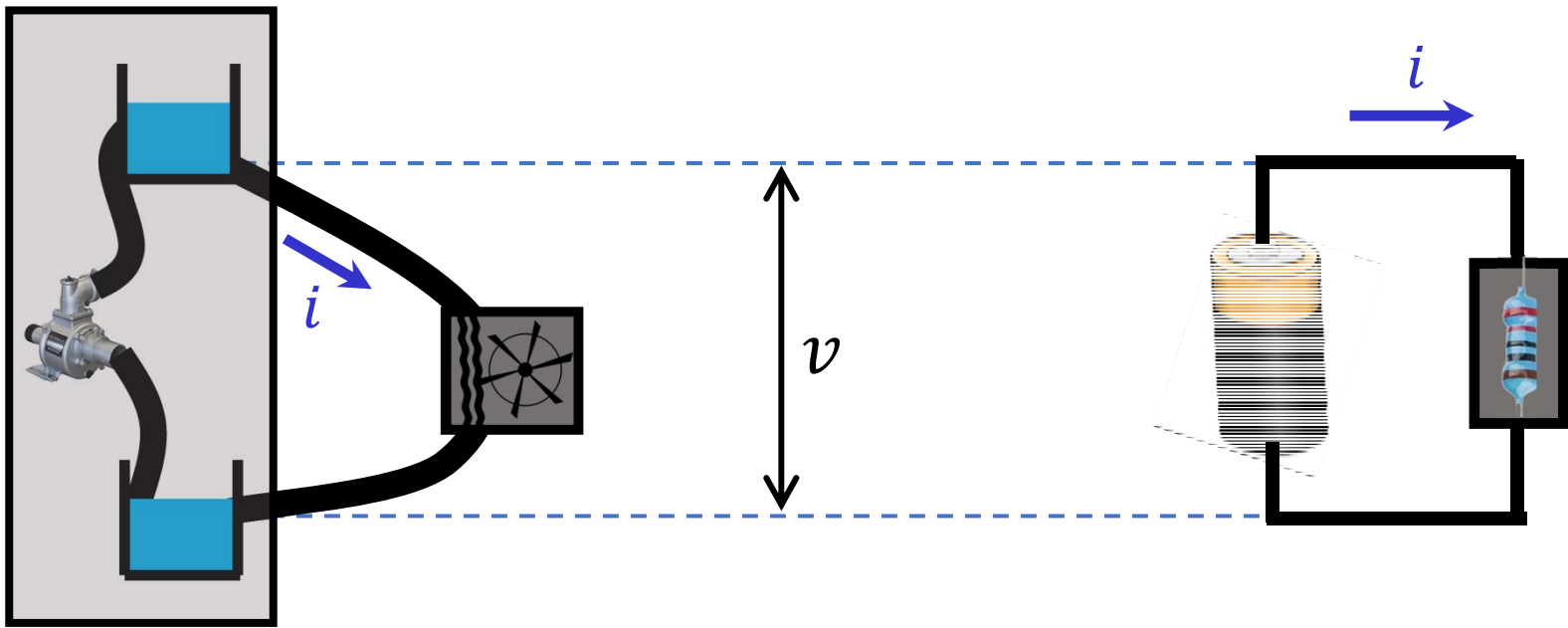


$$v_S = v_1 + v_2$$

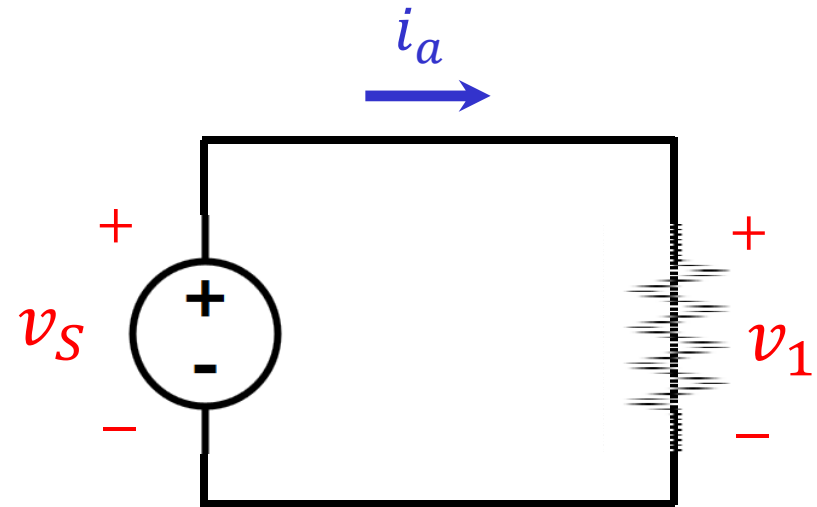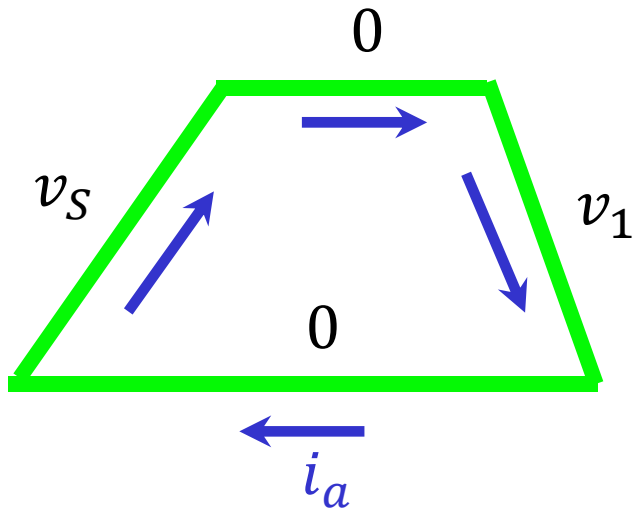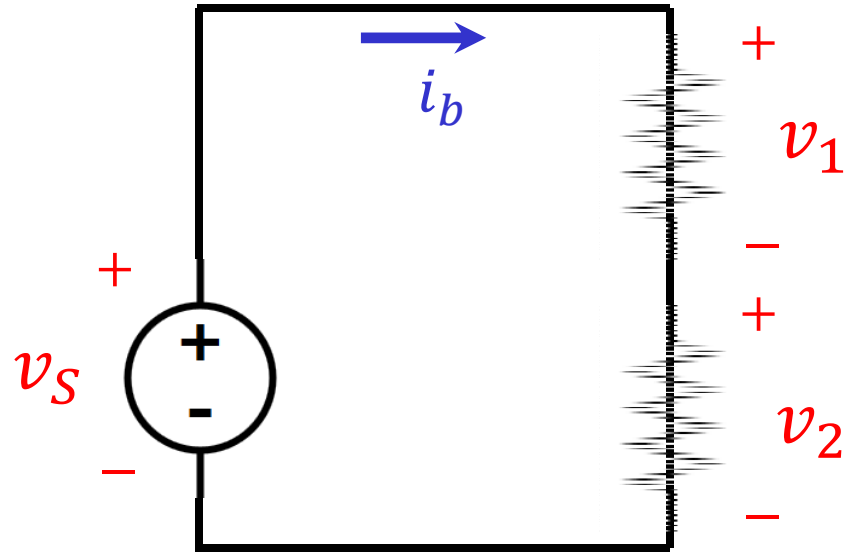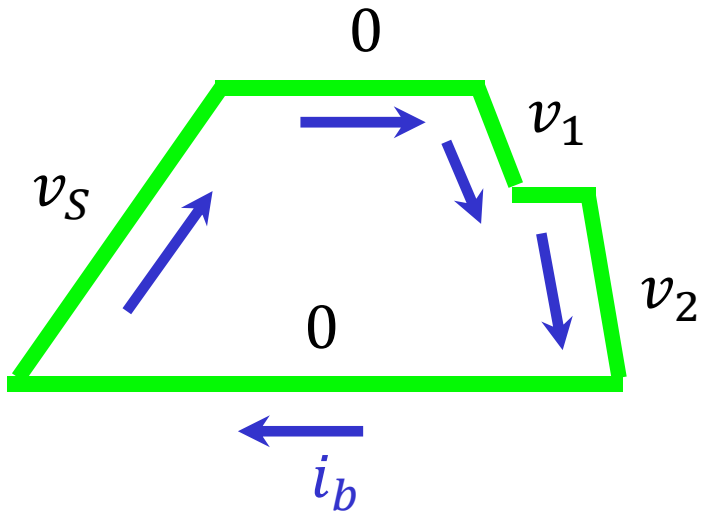


$$v_S = v_1$$



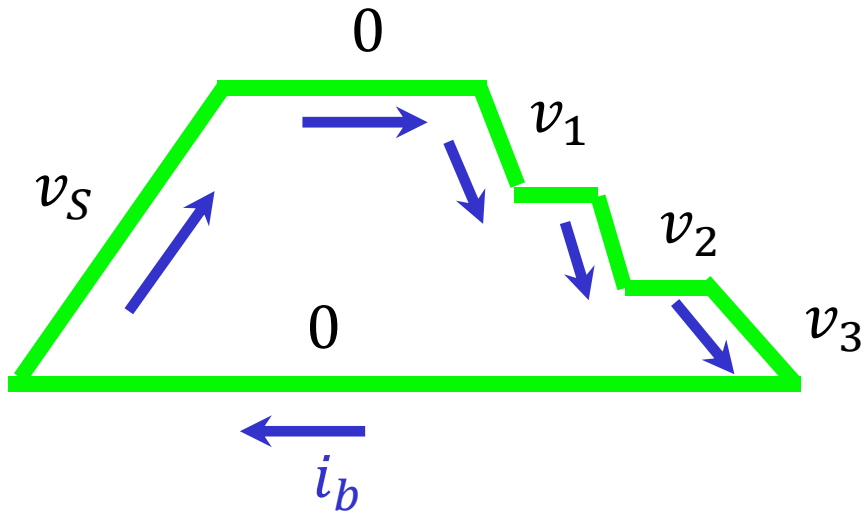


$$\sum_{up} v = \sum_{down} v$$

KVL  
Kirchhoff's Voltage Law

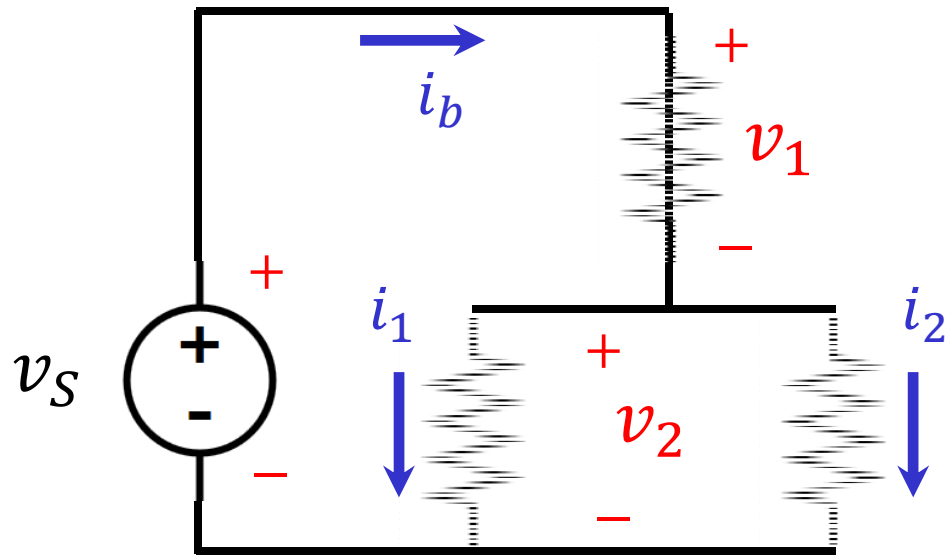



$$i_b = i_1 + i_2$$

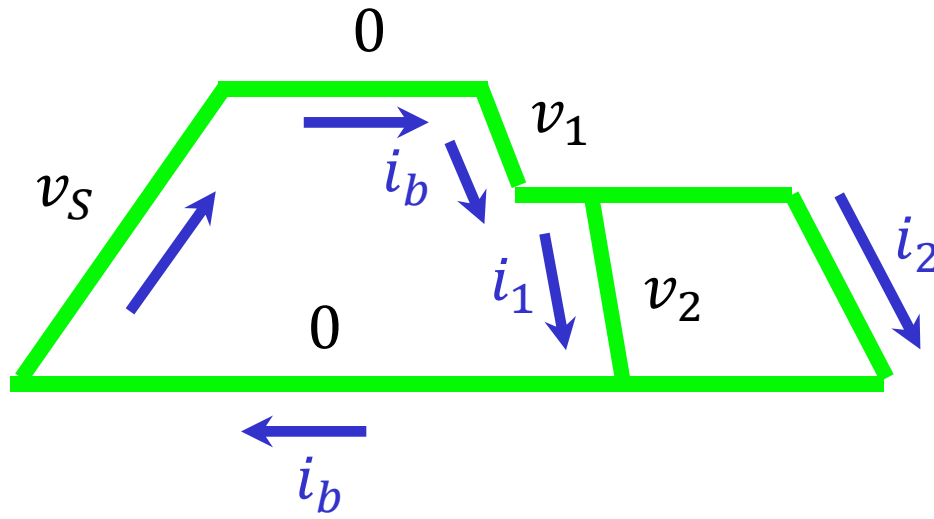

$$\sum_{in} i = \sum_{out} i$$

KCL  
Kirchhoff's Current Law

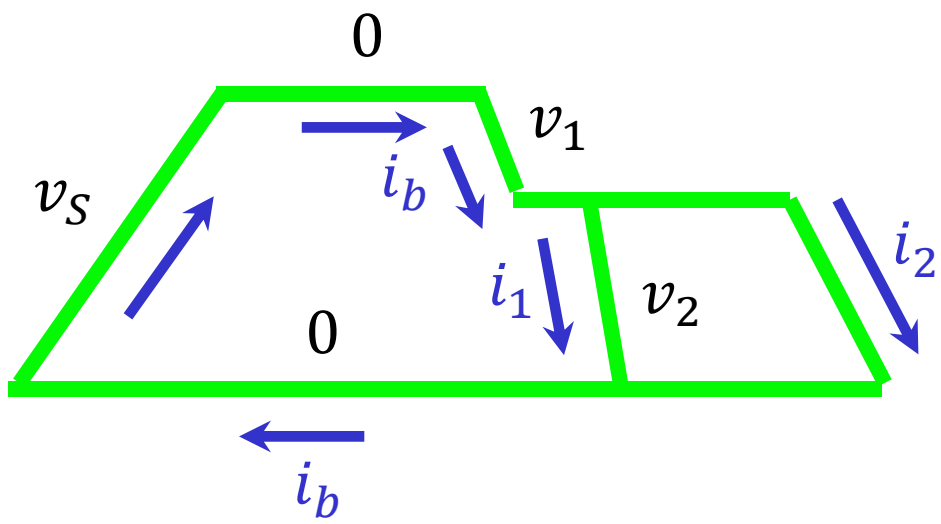


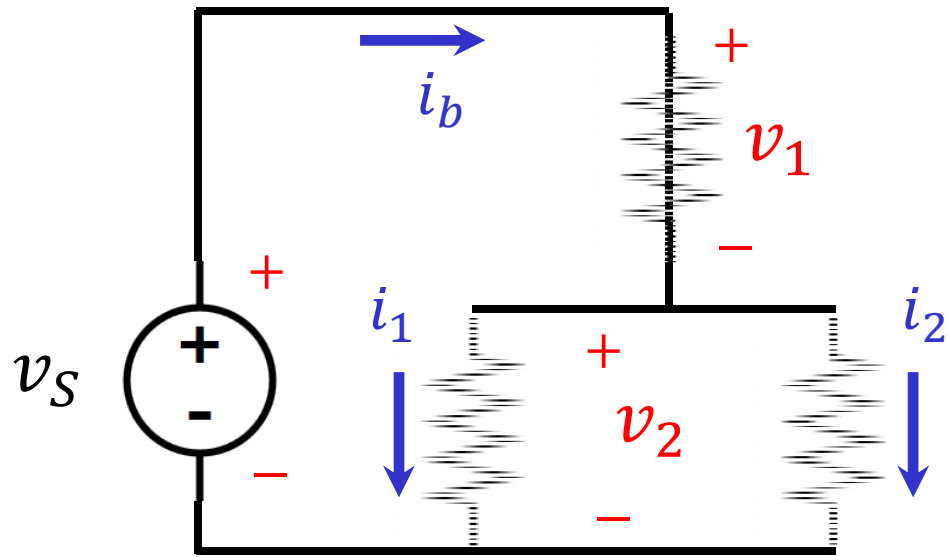


$$v_S = v_1 + v_2$$

$$i_b = i_1 + i_2$$


Relationship  
between  $i$  and  $v$  ?

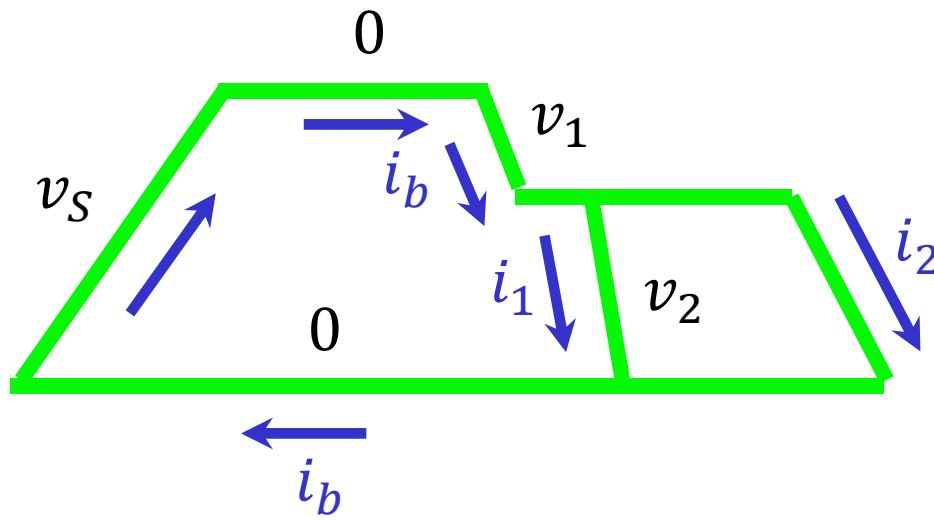

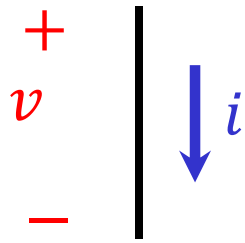


$$v = 0$$

$$R = 0$$

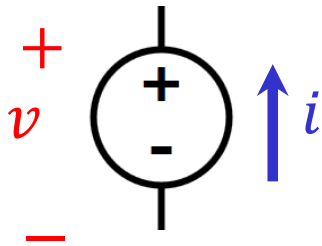


$$v = V_S$$

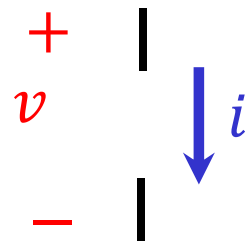

$$i = 0$$

$$R = \infty$$

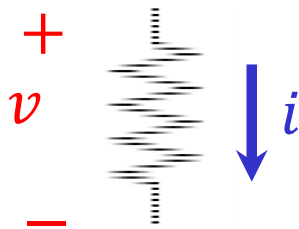

$$v = i \cdot R$$

$$i = \frac{v}{R}$$


Ohm's Law

Resistor

Symbol:  $R$

Unit: ohm ( $\Omega$ )

For example: 1 k $\Omega$

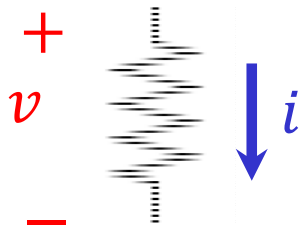


$$v = i \cdot R$$

$$i = \frac{v}{R}$$

Ohm's Law

Other components

$$v = f(i)$$

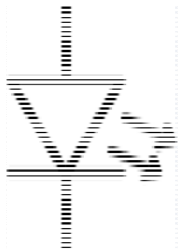

LED

$$v = V_{FIXED}$$

if it is on ( $i > 0$ )





Photocell

$$v = i \cdot R$$


$R(light)$

Rules of the game

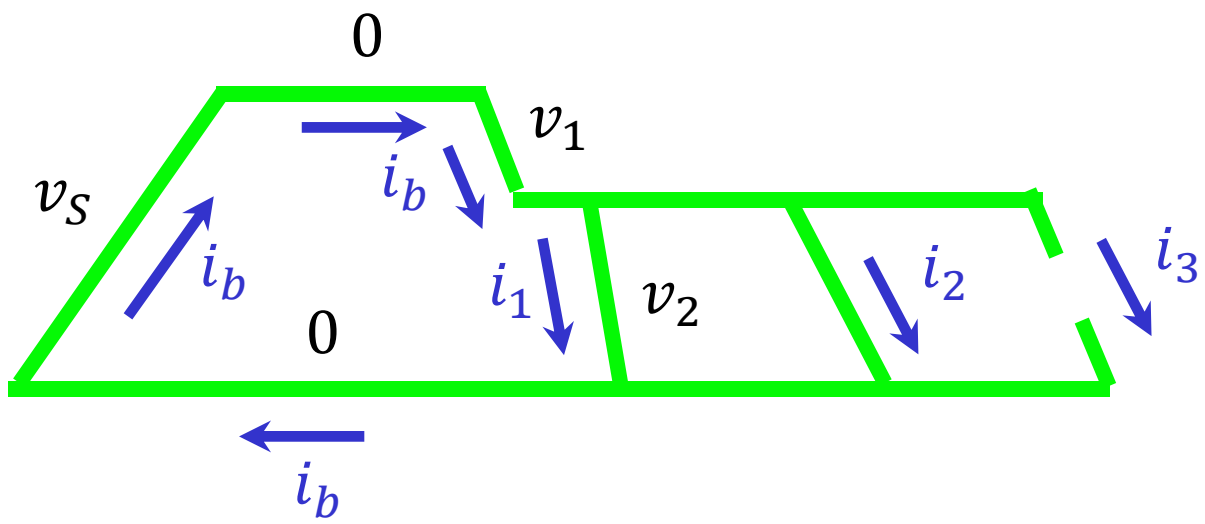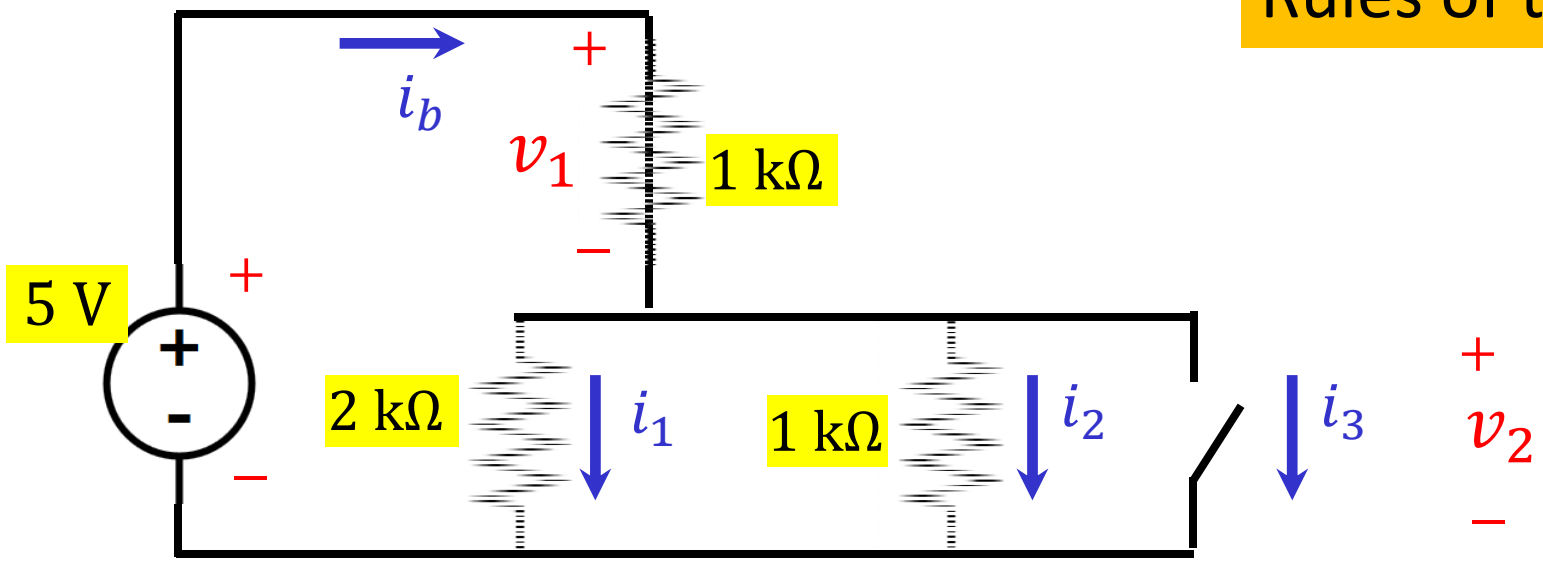



# Rules of the game

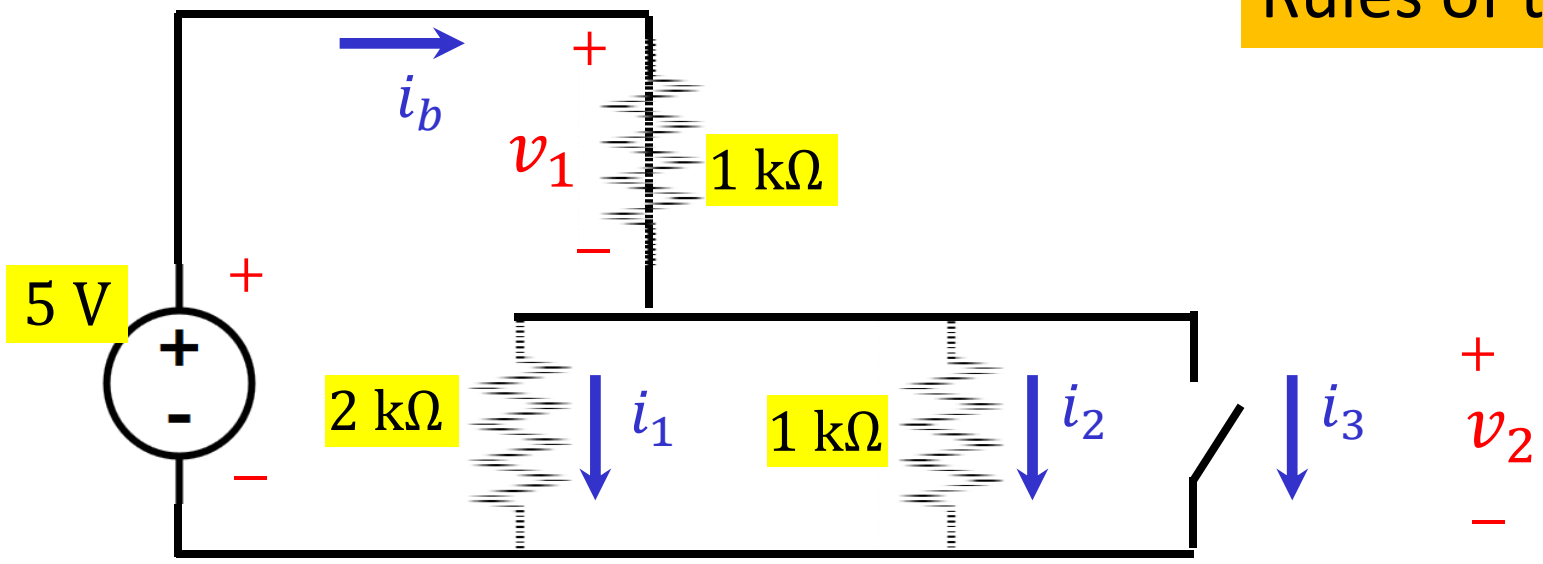

## KCL

$$\sum_{in} i = \sum_{out} i$$


## KVL

$$\sum_{up} v = \sum_{down} v$$
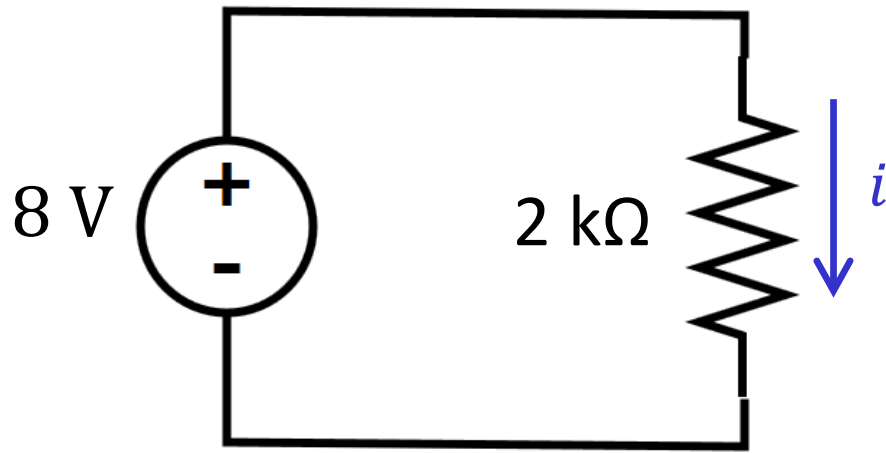
## Ohm's Law


$$v = i \cdot R$$

If the resistance  $R$  is  $2\text{ k}\Omega$ ,  
the current  $i$  is:





- [A] 0 mA
- [B] 2 mA
- [C] 4 mA
- [D] 16 mA
- [E] I don't know

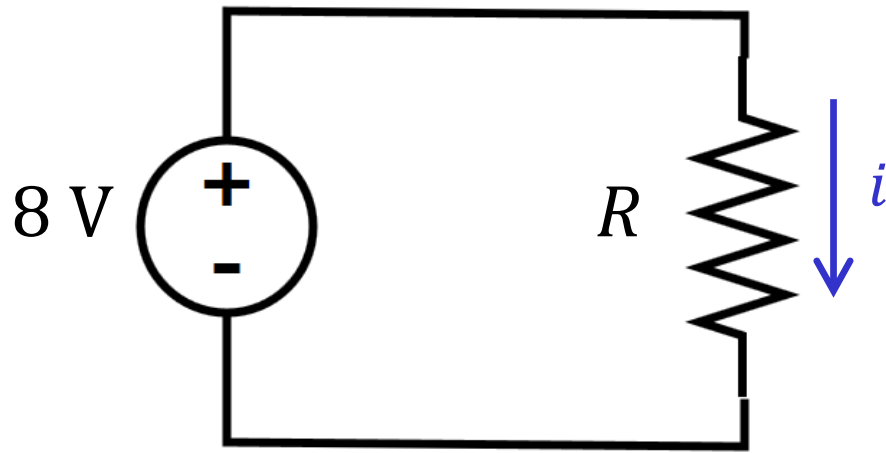What happens when the resistance  $R$  is lowered?




- [A] The current  $i$  increases
- [B] The current  $i$  decreases
- [C] The current  $i$  stays the same
- [D] The current  $i$  cannot be calculated
- [E] I don't know

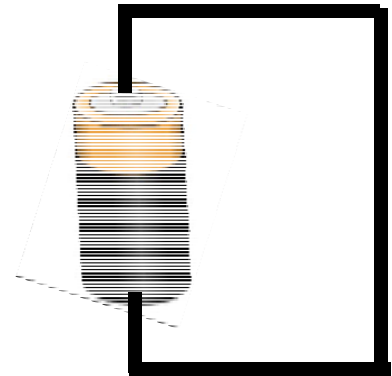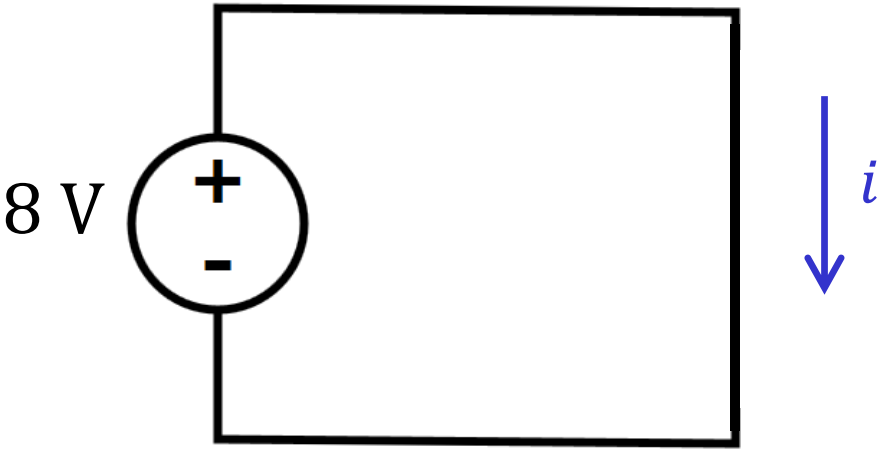What happens when the resistance  $R$  is lowered?





Very bad!

What is the current  $i$  ?

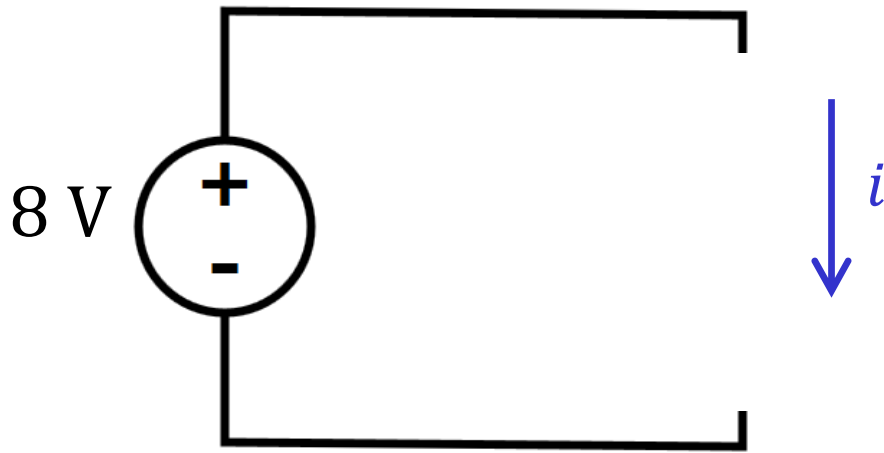


- [A] 0 mA
- [B] 8 mA
- [C] 8 A
- [D]  $\infty$
- [E] I don't know

What is the current  $i$  ?

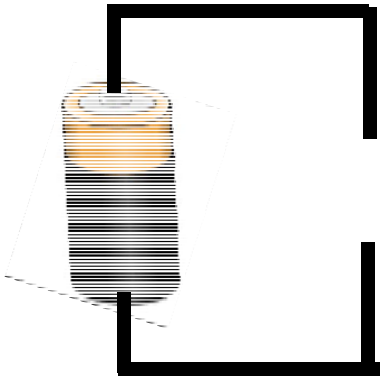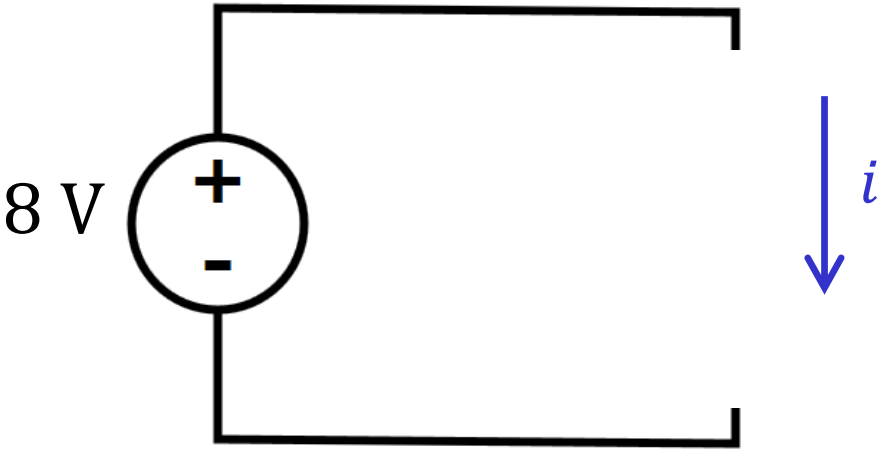




No current

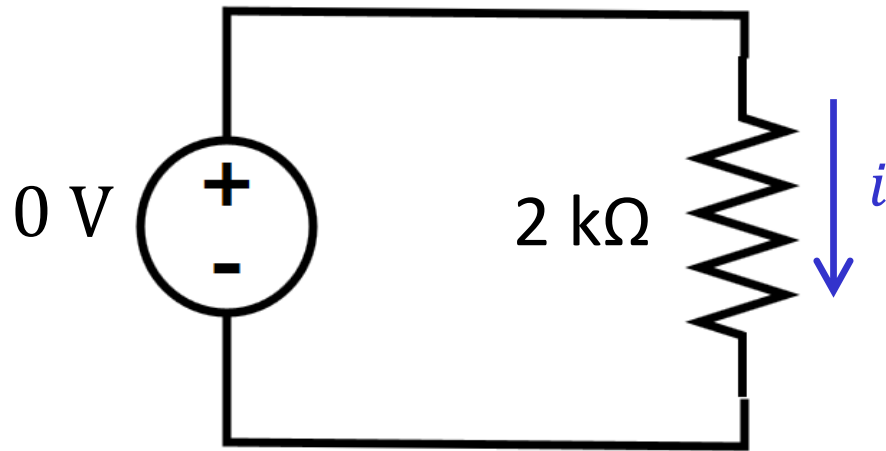If the resistance  $R$  is  $2\text{ k}\Omega$ , the current  $i$  is:




- [A] 0 mA
- [B] 2 mA
- [C] 4 mA
- [D] 16 mA
- [E] I don't know

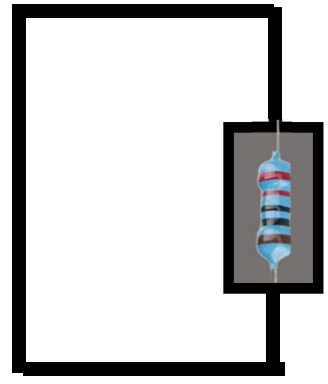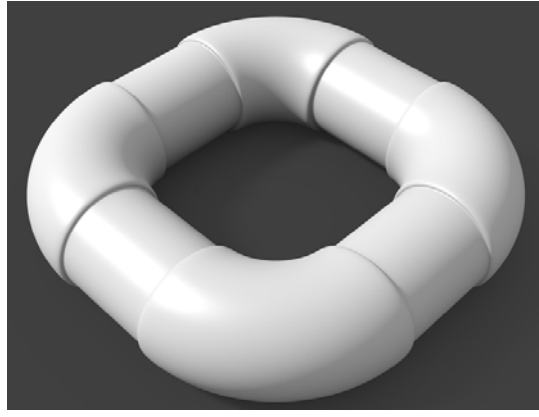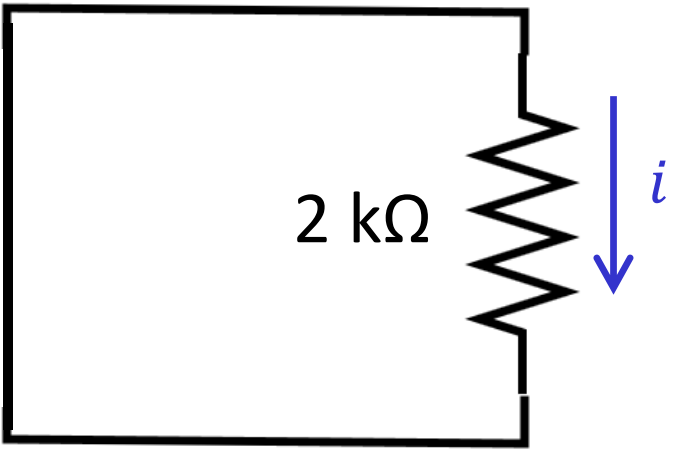If the resistance  $R$  is  $2\text{ k}\Omega$ , the current  $i$  is:




No current



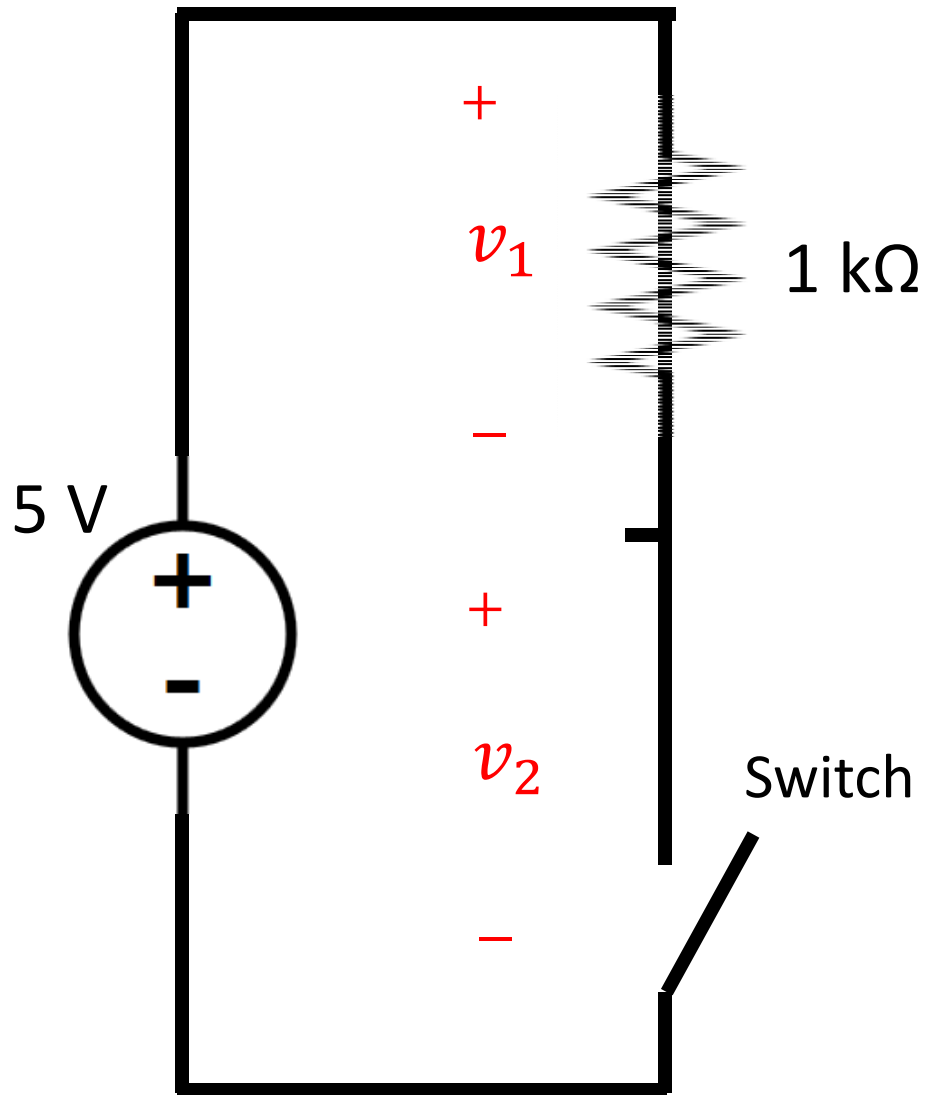

When the switch is open, the voltage  $v_2$  is:

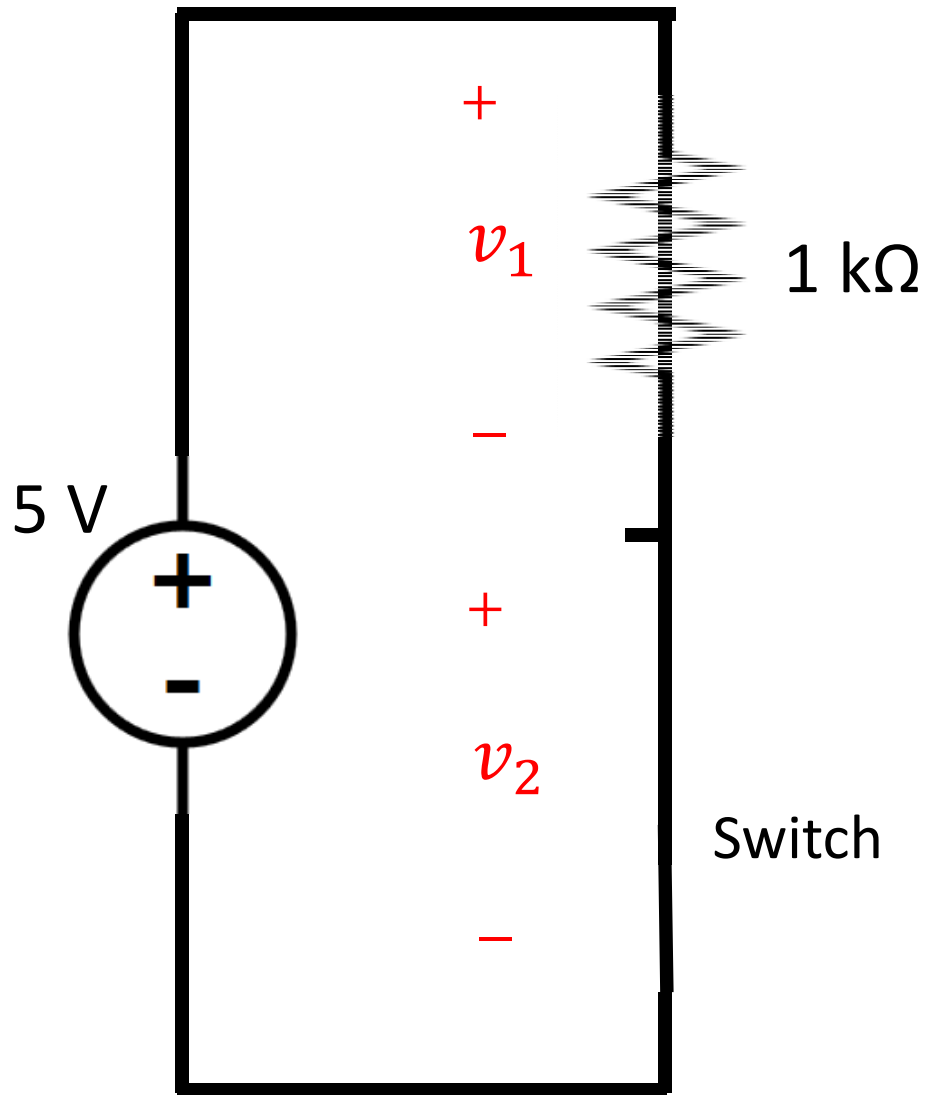- [A] 0 V
- [B] 1 mV
- [C] 1 V
- [D] 4 V
- [E] 5 V



When the switch is open, the voltage  $v_2$  is:

- [A] 0 V
- [B] 1 mV
- [C] 1 V
- [D] 4 V
- [E] 5 V

